

J-K Flip-Flop

Joshua Gould

12/5/2018

ECE 09.414 VLSI Design

Dept. of ECE

Henry M. Rowan College of Engineering
Rowan University

Outline



- J-K Flip-Flop Overview / Description
- Features / Problems
- Block Diagram
- Truth Table
- Master Slave Design
- Design Choices
- Logical Design
- Worst Case Design
- Logical Effort, Number of Stages, Delay
- Gate Sizes for Optimized Design
- Standard Cell Library & Layout Simulations
- Conclusion

Overview

JK Flip-Flop with Clear


- like the SR flip-flop, includes a "toggle" function when inputs are set to 1.
- Outputs only change with a clock pulse (Synchronous)
- J (set) and K (reset)
 - In other words:
 - J=1, K=0 sets the flip-flop
 - J=0, K=1 resets the flip-flop
 - J=1, K=1 toggles the flip-flop

Block Diagram

  


Input			Output		Description
J	K	C	Q	\bar{Q}	
0	0	0	0	0	Memory No change
0	0	0	0	1	
0	1	0	1	0	Reset Q >> 0
0	1	0	1	1	
1	0	0	0	0	Set Q >> 1
1	0	0	0	1	
1	1	0	1	0	Toggle
1	1	0	1	1	
x	x	1	0	1	Clear

Master/Slave Flip-Flop

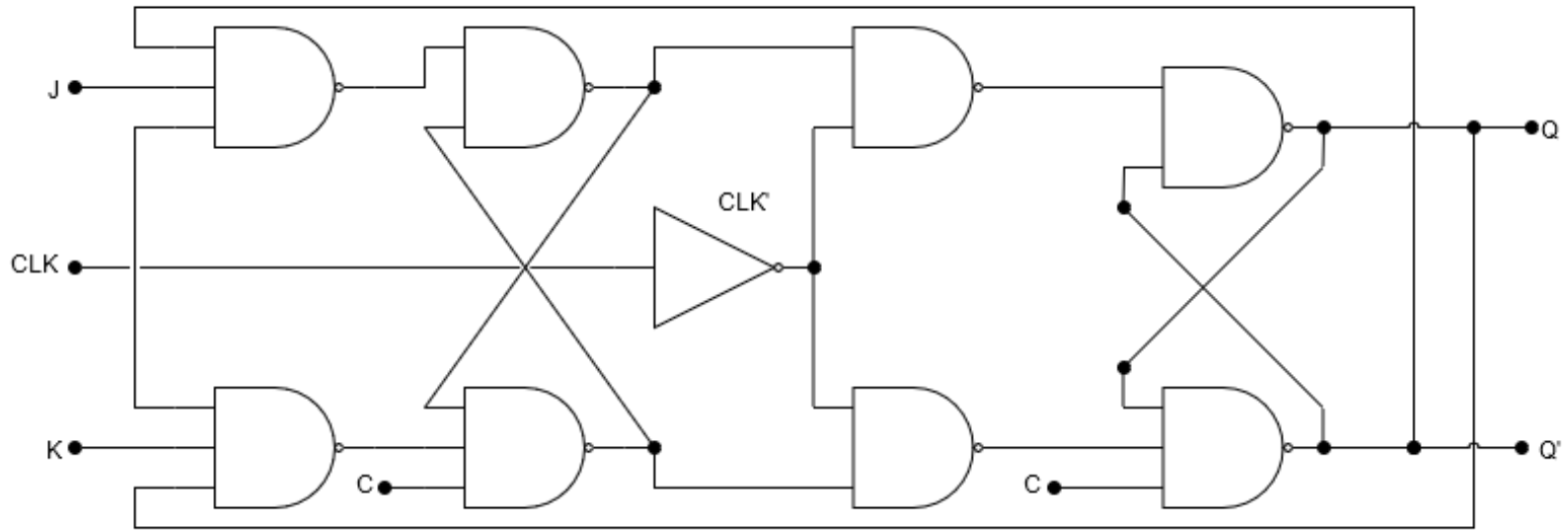



- Single flip-flops suffer from “race” timing problems
- Race timing occurs if the output Q changes state before the timing pulse of the clock input has time to go “OFF”.

Master/Slave Flip-Flop


 


- Two latch stages in a cascaded configuration
- Activated with opposite clock phases
- Eliminates uncontrolled oscillations since only one stage is active at any given time

Master/Slave Flip-Flop

  

  - Uncontrolled toggling when clock is high



- Slave toggles half a clock cycle after the master latch

Design Overview

- POSSIBILITY 1: Simple NAND Logic Gate
 - PROS:
 - Simple design
 - Small design area
 - Easily understandable
 - CONS:
 - Some constraints on the clock pulse width
 - Minimized features
 - 32 Transistors Required

Design Overview


- POSSIBILITY 2.1: Edge Triggered NAND-NOR

- PROS:

- Edge-triggered
 - Easily understandable

- CONS:

 - Inputs must be stable for some time before clock goes low.
 - Larger design area than NAND only (+2 NOR +2 NOT)
 - 44+ Transistors Required (Highest)
 - Timing is slower



Design Overview


- POSSIBILITY 2.2: LS73A Based

- PROS:

- Edge-triggered
 - Professional Based
 - Fast Switching


- CONS:

 - Inputs must be stable for some time before clock goes low.
 - Larger design area than NAND only (+4 AND +8 NOT)
 - Timing is slower
 - Power consumption is higher



Design Overview

- POSSIBILITY 3: Pass Transistors

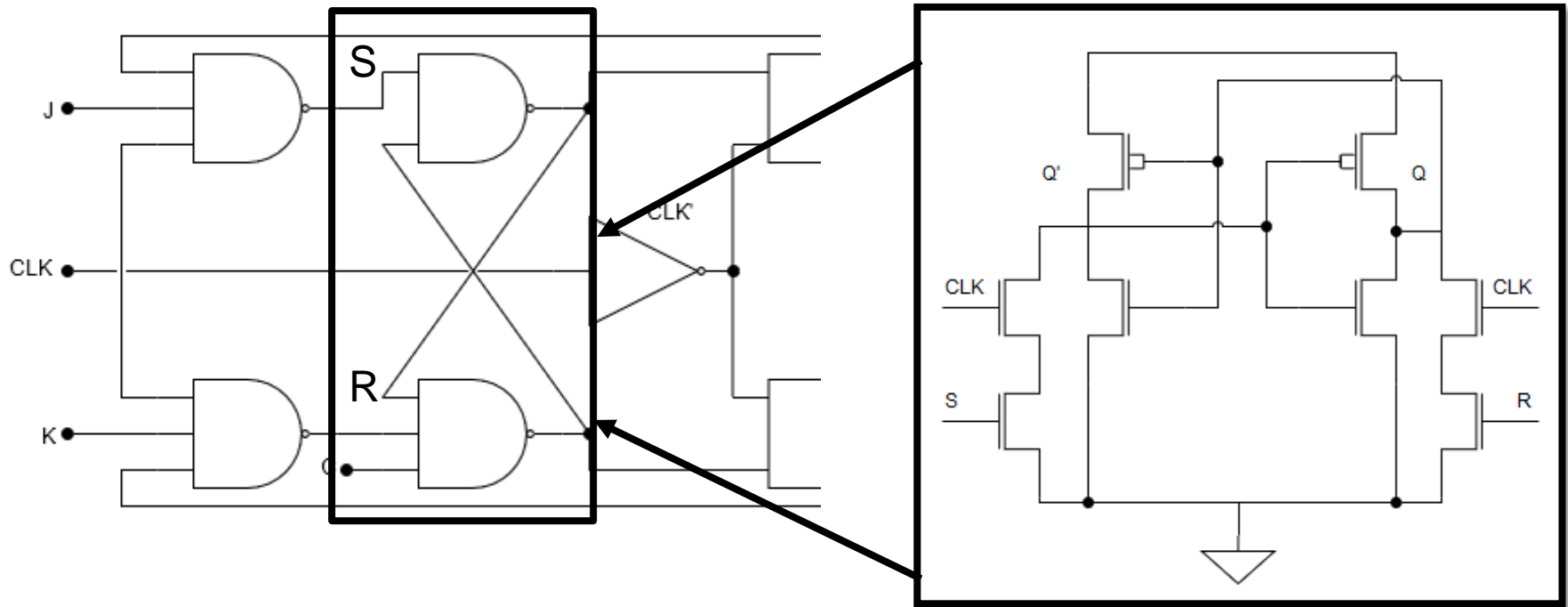

Design Overview


- POSSIBILITY 3: Pass Transistors

- PROS



- 18 Transistors
 - Smallest Logic Area

- CONS

 
- Additional components in latch area
 - Bad for pull-up level




Logic Design

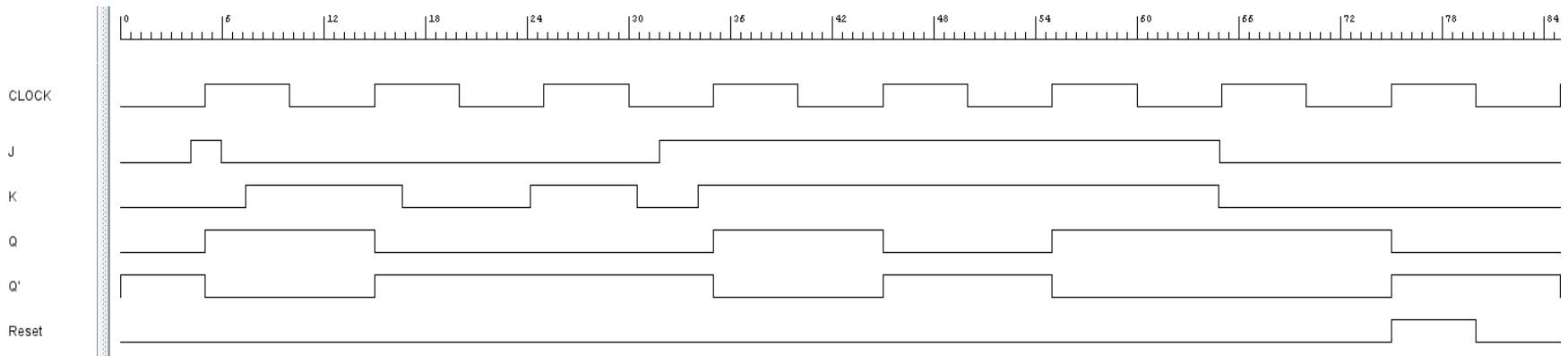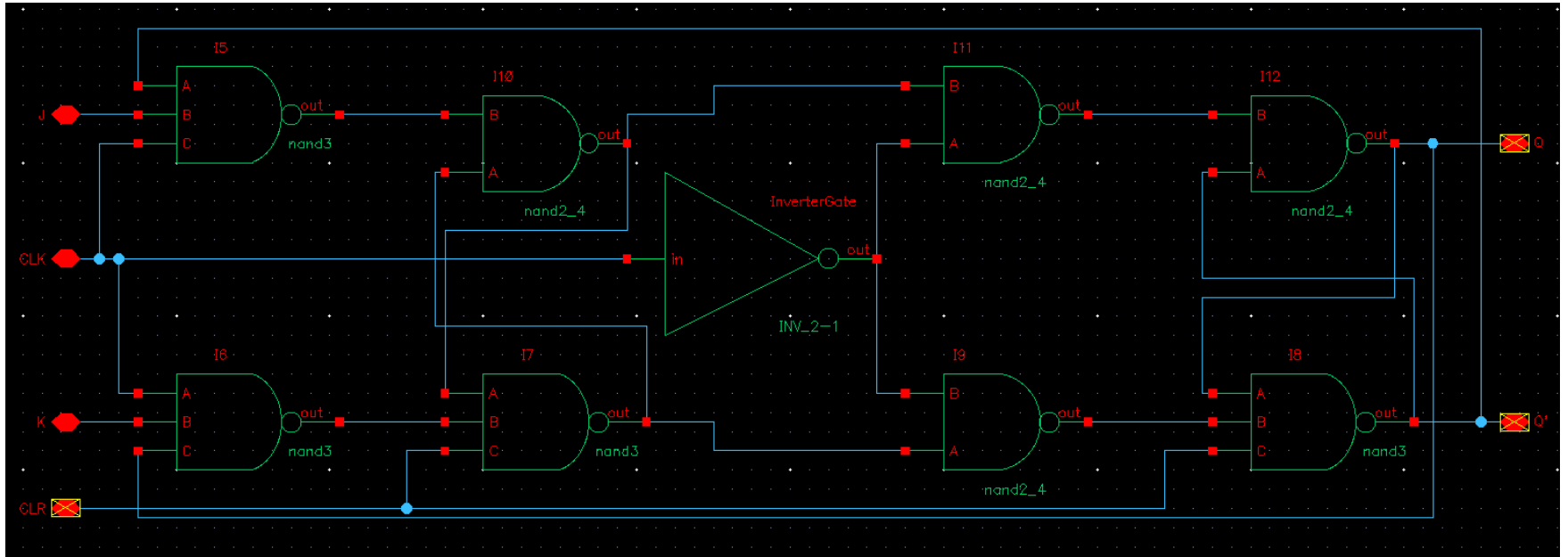

Transistor Design

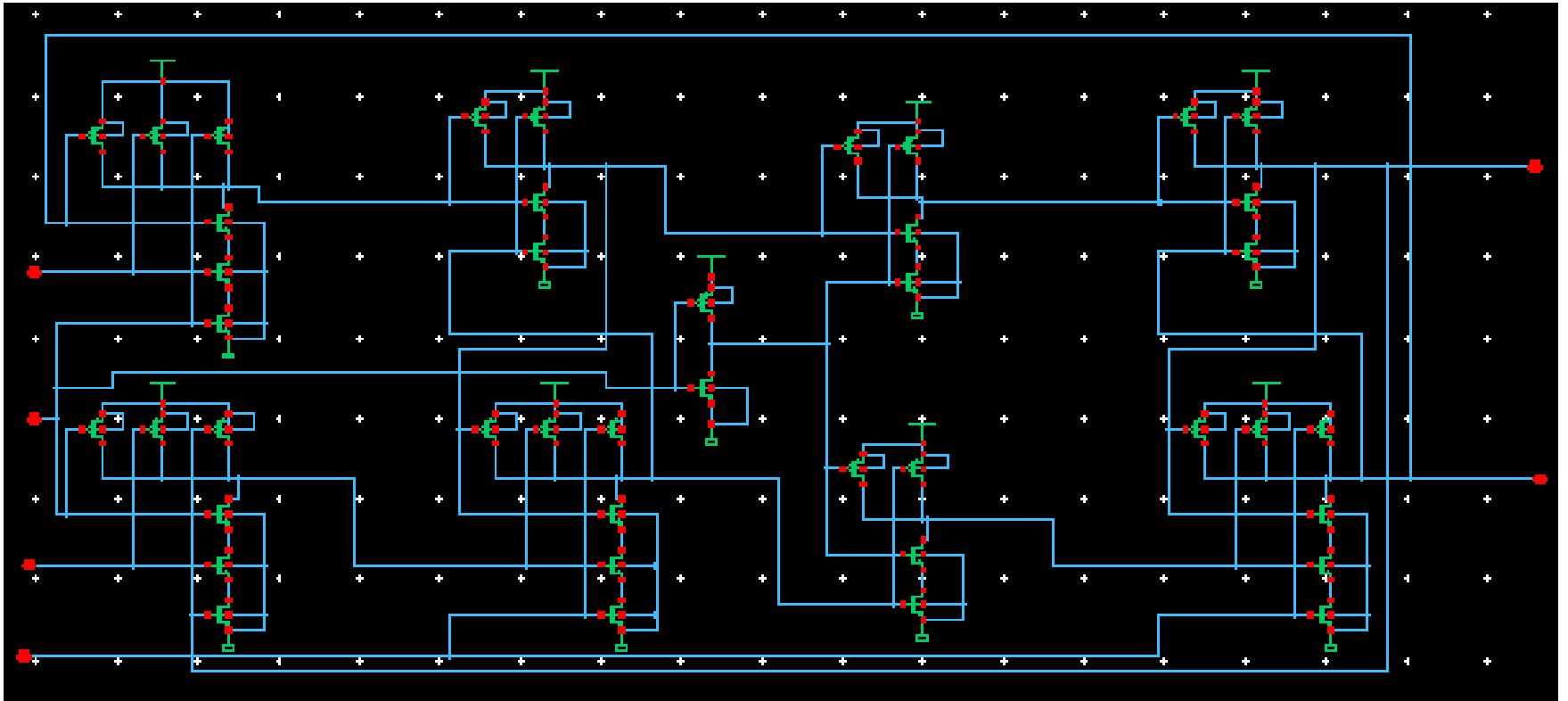

Worst Case Logical Path

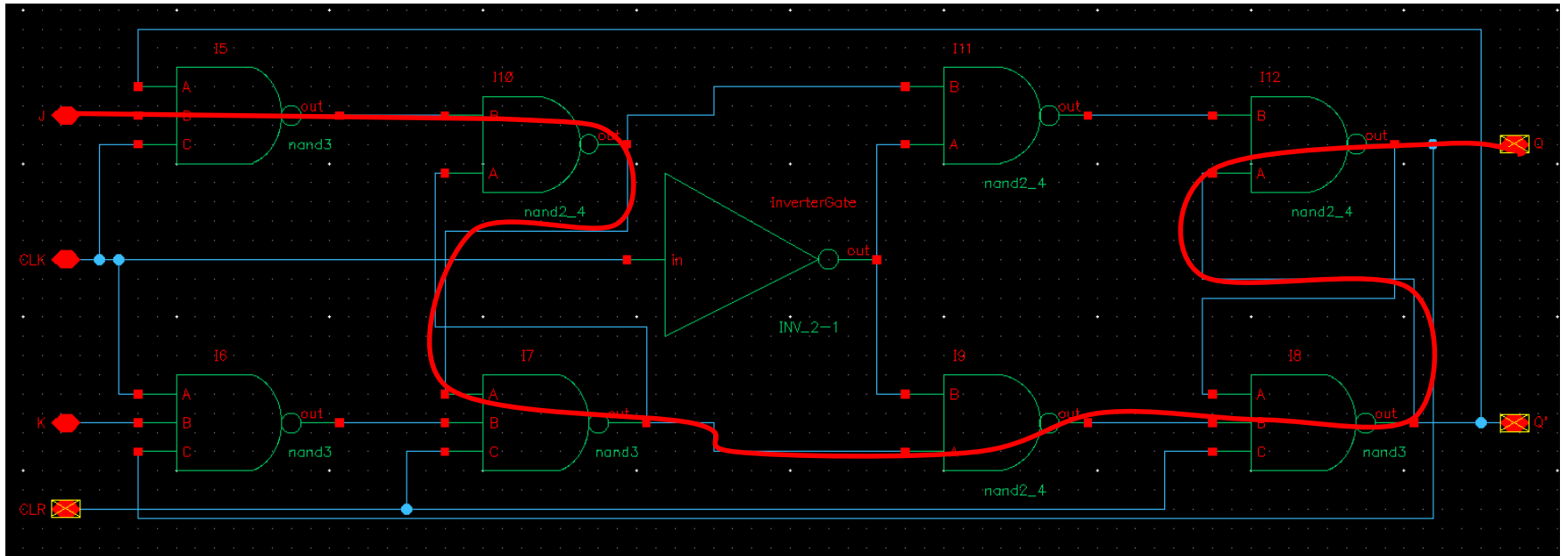

Logical Effort, Number of Stages, Delay

Variable	Stage				N = 4
	1	2	3	4	Path
b	1	2	1	3	B = 6
g	5/3	5/3	4/3	4/3	G = 400/81
h	0.364	0.364	0.455	0.455	H = 90/3 = 30
p	3	3	2	2	P = 10
$\hat{f} = F\overline{N}^1$	5.46	5.46	5.46	5.46	F = GBH = 888.88

$$D = N\hat{f} + P = 4 * 5.46 + 10 =$$

Spreadsheet Comparing Different Designs

Gate Sizes for Optimized Design

R	9.828
S	32.197
T	131.84
U	21.978

Standard Cell Library

Standard Cell Library Layouts

Standard Cell Library Extracted Layouts

Standard Cell Library Simulation

“Spectre” Netlist

Standard Cell Library Simulation

Input / Output Waveforms

Snap-together Standard Cells Circuit Layout

Snap-together Standard Cells Simulation

Input / Output Waveform

Delay Comparison

Logical Effort vs. Spectre

Conclusions